DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE Summer WANDED EXAMINATION - Control Engineering B. Tech Course in Electrical Engineering

	B. Tech Course in Electrical Engineering	
26	SEMESTER - I May 2015 Subject: Introduction to Electrical Engineering	
	Nay 2015 Subject: Introduction to Electrical Engineering Time: 3 Hours	$\mathbf{N} \mathbf{A}_{n-1}$, $\mathbf{N} \mathbf{A}_{n-1}$, $\mathbf{T} \mathbf{A}_{n-1}$
	CTION TO CANDIDATES:	Max. Marks: 70
	Attempt question No. 1	
	Attempt any five questions from the remaining	
	Assume suitable date mentioning clearly if necessary	
A	Answer the questions in sequential manner	
	and the questions in sequential mainter	
O.No.1)	Any Five;	
i)	One unit of electric energy means	(10)
ii)		
		and and
	materials.	
iii)	The unit of mechanical power is and to	rque is
iv)	According to steirnentz's law the hysteresis loss in a given by the expression	magnetic material is
V)	Transformer is device and works on	the principle of
vi)	For a given load if reactive power is low, be	power factor will
Q.No.2)		
a) B	riefly discuss contribution of following scientist to the ngineering; ii. Fleming and the law introduced by him v. Ampere	
c) E	xplain with neat sketch working of solar water heating systexplain with neat sketch working of solar photo voltoplications	em aic system and its
Q.No.3		(12)
a) O	btain an expression for the equivalent resistance of network (i) series and (ii) Parallel	when it is connected
	stablish relationship between;	
	i. Horse power and kW	
	ii. kW and kcalories	
ac	bulb rated 110V, 60 w is connected with another bulb records 220 V mains. Calculate the resistance which is require rallel with the first bulb so that both the bulbs may take their	d to be connected in

- a) For a R-L-C series circuit Obtain an expression for resonating frequency. Hence draw resonance curve, define bandwidth and Q factor.
- b) A series circuit consists of R=50 Ohm, L=0.1H and C=50µf connected across a single phase 230 V, 50Hz, supply. Calculate current drawn by the circuit, the p.f of circuit and its natue. Also calculate total power consumption and draw phasor diagram.
- c) State active, reactive and apparent power. Draw the power triangle stating terms of significance.

Q.No.5

- a) Show that the power supplied by star and delta connected three phase system remains the same
- b) Compare the single phase and three phase system of power supply
- c) There similar coils each of R=20 ohm, L=0.5H are connected (i) in star (ii) in delta to a three phase 400 V 50 Hz between lines. Calculate the line current and total power absorbed.

Q.No.6

- a) Draw a neat sketch of an ideal magnetic circuit and define the six significant terms related to the circuit.
- b) What is magnetic hystersis? Explain an experimental procedure for obtaining hysteresis loop and mark all points on it. (04)
- c) A steel ring of 10 cm mean radius and of cross section 1 cm in radius has an air gap of 1mm length. It is wound uniformly with 500 turns carrying current of 3 Amp. Find the total reluctance if air gap takes 60% of total m.m.f.

Q.No.7 (12)

- a) What is transformer? Explain construction and working of the single phase transformer, hence show that working flux always remains constant.
- b) Name different types of conductors used for power transmission purpose with their properties.
- c) Discuss different types of line supports used for power transmission along with their chief requirements.

Q.No.8 (12)

a) Name different soft wares used in engineering design.

b) Briefly discuss important features of MatLab for electrical engineering applications.